

[MEAE<sub>R</sub>]

INTEGRATED MASTER'S DEGREE IN AEROSPACE ENGINEERING

# LABORATORY 1

## LINEAR CIRCUIT ANALYSIS

March 24, 2021

**Group 1:**

António Nunes, 95770  
Francisco Branco, 95788  
Pedro Alves, 95836

**Professor:** José Teixeira de Sousa

# Contents

<b>List of Tables</b>	<b>1</b>
<b>List of Figures</b>	<b>1</b>
<b>1 Introduction</b>	<b>2</b>
<b>2 Theoretical Analysis</b>	<b>3</b>
2.1 Nodal Analysis . . . . .	3
2.2 Mesh Analysis . . . . .	4
2.3 Relationship between both methods . . . . .	6
2.4 Modified Nodal Analysis (MNA) . . . . .	6
2.5 Results . . . . .	7
<b>3 Simulation Analysis</b>	<b>8</b>
3.1 Operating Point Analysis . . . . .	8
<b>4 Final Conclusion and General Notes</b>	<b>9</b>

## List of Tables

1	Data used . . . . .	7
2	Results using Nodal Analysis . . . . .	7
3	Results using Mesh Analysis . . . . .	7
4	Simulation of Currents and Voltages . . . . .	8

## List of Figures

1	Linear Circuit with Resistors, Dependent and Independent Sources. . . . .	2
2	Node Numbering . . . . .	3
3	Mesh Numbering . . . . .	5
4	Circuit with Dummy Voltage Source . . . . .	8

# 1 Introduction

The aim of this laboratory assignment is to study the behaviour of a circuit containing exclusively linear components. In Figure 1 the stated circuit is presented. Despite being a simple circuit, it is a perfect example since our ultimate goal is to experiment some important Circuit Theory analysing tools, presented in Section 2, so that software simulation and theoretical analysis can be stacked up against each other more easily.

In Section 2, a theoretical analysis of the circuit is presented, both by the Node Analysis (2.1) and Mesh Analysis (2.2) methods, giving us some insights on different, although equivalent forms of exploring a linear circuit. In Section 3, the circuit is analysed by computational simulation tools, via *Ngspice*, and the results are compared to the theoretical results obtained in Section 2. The conclusions of this study are outlined in Section 4.

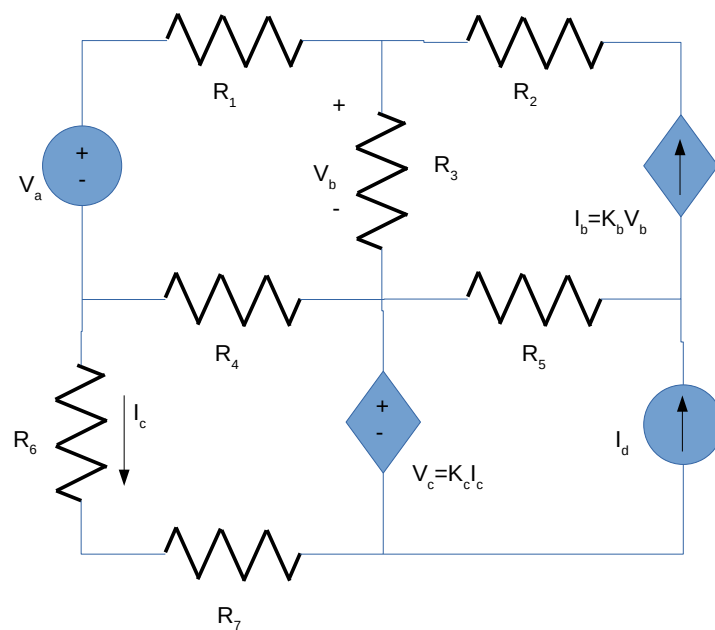


Figure 1: Linear Circuit with Resistors, Dependent and Independent Sources.

## 2 Theoretical Analysis

In this section, the circuit shown in Figure 1 is analysed theoretically using two methods: Nodal and Mesh Analysis.

### 2.1 Nodal Analysis

Before applying the method, it is important to discuss how it works. In general, it consists of discovering the voltages associated with each node of the circuit - they are the unknown variables in our equations. To obtain those, one has to apply *Kirchhoff's Current Law* (KCL) to the nodes, always having in mind that nodes on the ends of branches containing Voltage Sources cannot be analysed in this way.

In order to obtain a fully determined system of equations, we might need additional equations, *i.e.* equations derived from the circuit by inspecting. If we apply this method to the circuit in question, we end with 4 node equations, 1 supernode equation and 3 additional equations.

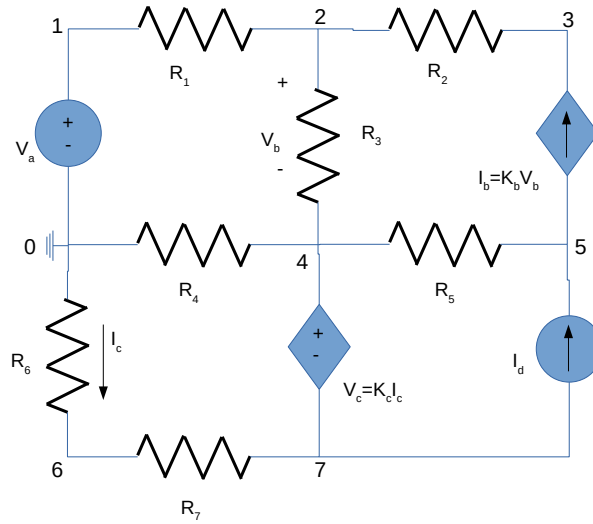


Figure 2: Node Numbering

The resultant system of equations, in the matrix and symbolic form is,

$$\begin{bmatrix} 1 & 0 & 0 & 0 & 0 & 0 & 0 \\ 0 & 0 & 0 & 1 & 0 & K_c G_6 & -1 \\ G_1 & -(G_1 + G_2 + G_3) & G_2 & G_3 & 0 & 0 & 0 \\ 0 & K_b + G_2 & -G_2 & -K_b & 0 & 0 & 0 \\ 0 & -G_2 & G_2 & -G_5 & G_5 & 0 & 0 \\ 0 & 0 & 0 & 0 & 0 & G_6 + G_7 & G_7 \\ 0 & G_3 & 0 & -(G_3 + G_4 + G_5) & G_5 & G_7 & -G_7 \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \\ V_3 \\ V_4 \\ V_5 \\ V_6 \\ V_7 \end{bmatrix} = \begin{bmatrix} V_a \\ 0 \\ 0 \\ 0 \\ I_d \\ 0 \\ I_d \end{bmatrix} \quad (1)$$

Where  $G_i \equiv$  conductance of the  $i^{th}$  resistor.

Since, for the Node Analysis method, the voltages used refer to the different nodes, we are free to set a reference point in whatever node we desire. Note that this has no real impact on the voltage drops on each component, since those are calculated by taking the difference of the nodal voltages on each of the component's ends. Doing so, we should clarify that the voltage

associated with the relative Ground (GND),  $V_0$ , was omitted from the matrix because it leads to a trivial relation:

$$V_0 = 0 \quad (2)$$

which can be directly substituted on the remaining equations. We could do the same for  $V_1$  but it feels unnecessary and would be making the other equations harder to decipher. That said, you can clearly see from the first line of the matrix that  $V_1$  is directly associated with  $V_a$ :

$$V_1 = V_a \quad (3)$$

An additional equation comes from

$$V_c = V_4 - V_7 = K_c I_c = K_c (-V_6) G_6 \implies V_4 + V_6 (K_c G_6) - V_7 = 0 \quad (4)$$

which corresponds to the second line of the matrix in 1.

The following 4 equations come from nodes 2, 3, 5, 6, respectively applying the linear relations described. The last equation is obtained from «merging» nodes 4 and 7, and comparing the currents that enter and exit this «supernode»<sup>1</sup>.

## 2.2 Mesh Analysis

In this second method, instead of looking for nodes, we are interested in meshes (as the method's name indicates).

Usually, we create *fictitious* currents in each mesh and we then apply *Kirchhoff's Voltage Law* (KVL) to either the individual meshes, or to a loop. This difference occurs because sometimes, analogously to the previous method, we are unable to provide an equation for a given mesh, specially if there are Current Sources involved.

In that case, one has to look for additional equations by, for example, attributing the values of known currents to *fictitious* ones. Another option is to analyse supermeshes, *i.e.* non-elementary loops, that avoid these components.

For the analysis in questions, we make use of 2 meshes, 0 supermeshes and 2 additional equations.

---

<sup>1</sup>Note that this is possible due to the linear properties of KCL

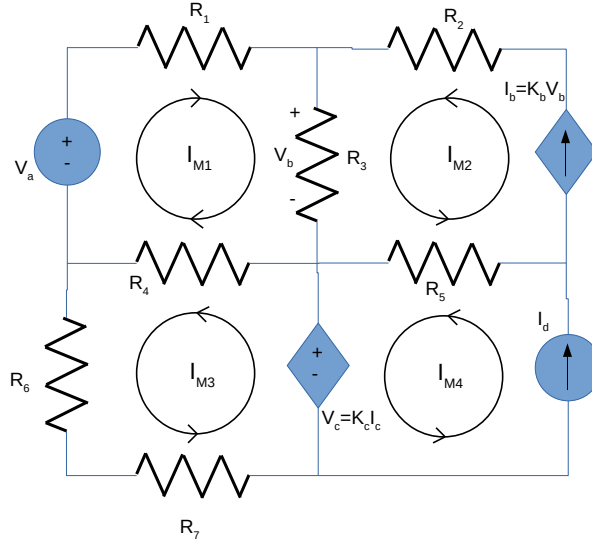


Figure 3: Mesh Numbering

Just with a glance we can realise that the equations provide a much smaller matrix, when compared to the previous one. This is expected since there is a greater number of nodes when compared to meshes (this phenomena is detailed in Section 2.3),

$$\begin{bmatrix} R_1 + R_3 + R_4 & R_3 & R_4 \\ -K_b R_3 & 1 - K_b R_3 & 0 \\ R_4 & 0 & (R_4 + R_6 + R_7 - K_c) \end{bmatrix} \begin{bmatrix} I_{M1} \\ I_{M2} \\ I_{M3} \end{bmatrix} = \begin{bmatrix} V_a \\ 0 \\ 0 \end{bmatrix} \quad (5)$$

where  $I_{M_i} \equiv$  the *fictitious* current on mesh  $M_i$ .

Above, we present a  $3 \times 3$  matrix, although it is simple to observe that the circuit has 4 meshes. We obviously omitted one *fictitious current* because it is trivial to conclude by inspection that the current that flows through Mesh 4 is actually the current from the current source  $I_d$ . So, the fourth equation would be:

$$I_{M4} = I_d \quad (6)$$

From applying KVL to meshes M1 and M3 one can easily define the first and third equations in matrix 5, respectively.

The second matrix equation comes from inspecting directly mesh M2.

$$I_{M2} = I_b = K_b V_b = K_b (I_{M1} + I_{M2}) R_3 \implies K_b R_3 I_{M1} + (K_b R_3 - 1) I_{M2} = 0 \quad (7)$$

## 2.3 Relationship between both methods

We should note that, while the methods used clearly differ in the way they're applied, they are, obviously, intimately connected and the results given by one can be derived from the other's.

For example, given the voltage values on each node from the Node Analysis, we can easily compute the voltage drops on each of the resistors and by applying *Ohm's* law, get the values of the current flowing through them. On the other hand, given the current values calculated with the use of the Mesh Analysis method, we can do the opposite to get the nodal voltages. An example is given in Section 2.5.

Since, for the voltage drops in each component, you need 2 values (one for each of the nodal voltages) it is easy to see that you'll quite surely end up with more equations, and thus a bigger matrix to solve, when doing a Nodal Analysis. However, as will be explained in greater detail in Section 2.4, a similar method is implemented by circuit solvers like *Ngspice*.

## 2.4 Modified Nodal Analysis (MNA)

One can see that it is trivial to find the meshes in a plane circuit. When it comes to the nodes, there can be an increment of complexity, even though it still doesn't offer much difficulty for humans.

However, *Ngspice*, and in general the majority of circuit simulators, prefers to analyse nodes rather than meshes. This occurs mainly for one reason. In a topological point of view, it is easier for machines and programs to identify nodes. The latter requires a level of processing higher than the first, which makes it a worse choice in most cases, increasing the complexity of tasks a computer needs to execute, and consequently the amount of processing time.

In spite of that, the choice of nodal analysis might bring problems as we saw previously, regarding the existence of Voltage Sources. Hence, the software adapts the nodal analysis by having a systematical method, in order to perform under any kind of circuit, what we call the *Modified Nodal Analysis*, or simply MNA.

It may be relevant to discuss briefly this method as it generated the results seen in Table 4.

Since in Nodal Analysis one cannot write equations for nodes connected to Voltage Sources using KCL, in MNA<sup>2</sup> we assign an unknown current to a voltage source, hence creating new unknowns. We also relate the voltage drop between nodes and voltage source imposed. We later apply KCL to all the nodes and solve the system. Some benefits to this method are that the computer doesn't need to compute any supernodes and in the final matrix we have results regarding both voltages and currents.

---

<sup>2</sup>Procedure seen in <https://www.swarthmore.edu/NatSci/echeeve1/Ref/mna/MNA2.html>, accessed on March 20th 2021

## 2.5 Results

In this last section we will discuss the results that the methods studied provided. The resolution of the equations on the matrix-form was done with the help of *Octave*.

The data used for solving the circuit was generated with the provided *Python* script, using the student number 95770, and can be found in the table below:

Name	Value [Units]
R1	1.03504497262 [ $k\Omega$ ]
R2	2.01159104669 [ $k\Omega$ ]
R3	3.03557466091 [ $k\Omega$ ]
R4	4.10235086526 [ $k\Omega$ ]
R5	3.09889833746 [ $k\Omega$ ]
R6	2.00952426524 [ $k\Omega$ ]
R7	1.04158528578 [ $k\Omega$ ]
Va	5.22552047598 [V]
Kb	7.3172497028 [ $mS$ ]
Kc	8.09359354837 [ $k\Omega$ ]
Id	1.04791133328 [ $mA$ ]

Table 1: Data used

Name	Value [V]
V1	5.2255
V2	4.9893
V3	4.5085
V4	5.0219
V5	9.0099
V6	-2.0013
V7	-3.0387

Table 2: Results using Nodal Analysis

Name	Value [ $mA$ ]
$I_{M_1}$	0.22824
$I_{M_2}$	-0.239
$I_{M_3}$	0.99593

Table 3: Results using Mesh Analysis

For the Nodal Analysis (see subsection 2.1) it is pertinent to address that the solution is a matrix with an incredible amount of terms, so it would be almost impossible, if not painful, to insert the symbolic solution in the present document. The solutions, after substituting the values of the resistances and other constants (from Table 1) are presented in Table 2.

Analogously, for the Mesh Analysis (see Subsection 2.2) the results are shown in Table 3.

As stated in Section 2.3, one can verify the equivalence of both methods, with the use of *Ohm's Law*, calculating the current flowing through the resistors using the voltage drop from two consecutive nodes, from the Nodal Analysis, or doing the reciprocal: to derive the nodal voltages using the current from the Mesh Analysis. Here's an example of the equivalence cited using Ohm's Law:

$$0.2362[V] = V_1 - V_2 = R_1 I_{M_1} \iff I_{M_1} = \frac{V_1 - V_2}{R_1} = 0.2282[mA] \quad (8)$$

Bearing that  $V_1 - V_2$  is the voltage drop between  $R_1$ .

Doing the same for the rest of the components proves, somewhat, that both analysis lead to the same results. To confirm them completely, we should compare them to the real results obtained from the simulation that we're about to explore in Section 3. This comparison and verification can be found in the conclusion (Section 4).



### 3 Simulation Analysis

#### 3.1 Operating Point Analysis

In this section, the results given by the *Ngspice* simulation are presented in Figure 4. Table 4 shows the simulated operating point results for the circuit under analysis.

Name	Value [A or V]
@gb[i]	-2.38996e-04
@id[current]	1.047911e-03
@r1[i]	2.282360e-04
@r2[i]	-2.38996e-04
@r3[i]	-1.07597e-05
@r4[i]	1.224163e-03
@r5[i]	-1.28691e-03
@r6[i]	9.959274e-04
@r7[i]	9.959274e-04
v(1)	5.225520e+00
v(2)	4.989286e+00
v(3)	4.508524e+00
v(4)	5.021948e+00
v(5)	9.009942e+00
v(6)	-2.00134e+00
v(7)	-2.00134e+00
v(8)	-3.03868e+00

Table 4: Simulation of Currents and Voltages<sup>3</sup>

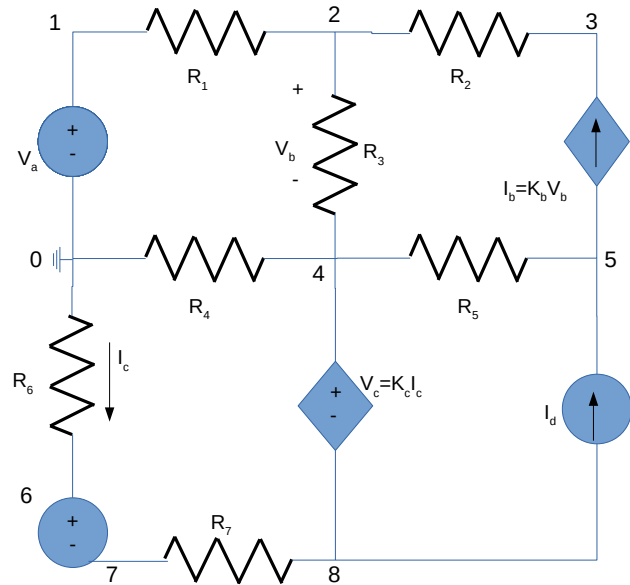


Figure 4: Circuit with Dummy Voltage Source

It should be stated that one node was added between resistors R6 and R7 in order to add a dummy 0V-voltage source in that location. This was done as a work-around the mechanics of *Ngspice*<sup>4</sup> to enable the voltage source  $V_c$  to be controlled by the current passing through  $R_6$ ,  $I_c$ , and has no real impact on the circuit itself since that, by definition an ideal voltage source has a  $0\Omega$  resistance, and so it doesn't change the current neither the voltage drop between the nodes. This is the reason why, on Table 4, we have v(6) and v(7) outputting the same value.

<sup>3</sup>Variables preceded by @ denote *currents* and are expressed in Ampere; the remaining variables are *voltages* and are expressed in Volt. Gb represents the voltage controlled current source.

<sup>4</sup>*Ngspice* software only accepts controlling currents that pass in a voltage source. In our example the controlling current  $I_c$  passes through a resistor.

## 4 Final Conclusion and General Notes

To conclude, we can realise that the results presented in Tables 2 and 3 are similar to the ones displayed in Table 4, with exception of the last represented decimal places (due to rounding), which is very satisfactory. Despite that, we must be more insightful and analyst towards the data given along this report.

So let us firstly discuss about the linearity of the circuit. Because all the components are linear, a steady-state solution is always expected, invariable with respect to time. Also, another consequence of this, is that we should not attend any "butterfly-effects", *i.e.* a little nuance in the given data should not scale up to enormous disparities in the outputs, which is one factor as to why the results fit so well with the simulation.

Secondly, it should be pointed out that although the circuit analysis is simple, the equations lead to complicated algebraic systems, which without *Octave* would be very time consuming and easy to miscalculate. The best evidence of that is the *symbolic* solution matrix from both matrix equations (1) and (5), which is not presented in this report due to its size and the complexity of each entry, as mentioned in Section 2.5.

Finally, as already discussed in previous Sections, because the simulation software uses MNA, an equivalent method as the ones used to analyse theoretically, the results of both approaches (theoretical and practical) must be the same. As an exercise, the circuit could also be analysed using the Superposition Theorem, its *Thévenin's* or *Norton's* equivalents and of course, we must expect no difference in the results. These analysis are beyond the extent of this report.

Overall, this project was a beneficial tool to develop our theoretical circuit analysis and software programming capabilities.